

Austin Smothers
Professor Bustamante
CSC 137
June 10, 2019

Chapter 2 Homework

2.1 Evaluate $f = x\overline{y} + yz$ for $x = 1, y = 0$, and $z = 1$ and for $x = 1, y = 1$, and $z = 0$.

$$x=1, y=0, z=1 \rightarrow 1.1 + 0.1 \rightarrow 1 + 0 = \mathbf{1}$$

$$x=1, y=1, z=0 \rightarrow 1.0 + 1.0 \rightarrow 0 + 0 = \mathbf{0}$$



2.2 Evaluate $y = \overline{_c}\overline{x} + _cx$ for $_c = 0$ and $x = 1$ and for $_c = 1$ and $x = 1$ where $_c$ is an active-low signal.

$_c$ = active-low signal inverter therefore 0=on 1=off



$$_c=0, x=1 \rightarrow 1.0 + 0.1 \rightarrow 0 + 0 = \mathbf{0}$$

$$_c=1, x=1 \rightarrow 0.0 + 1.1 \rightarrow 1 + 1 = \mathbf{1}$$

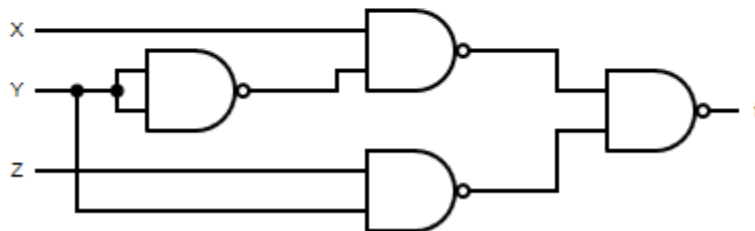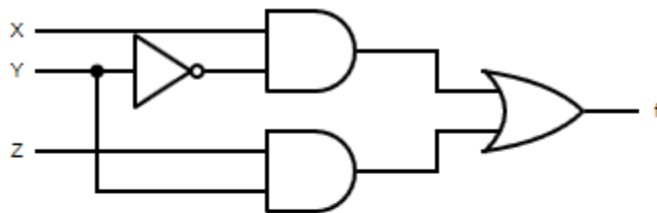2.5 Draw the circuit schematic for $f = x\overline{y} + yz$ and then convert the schematic to NAND gates using the steps illustrated in the textbook.



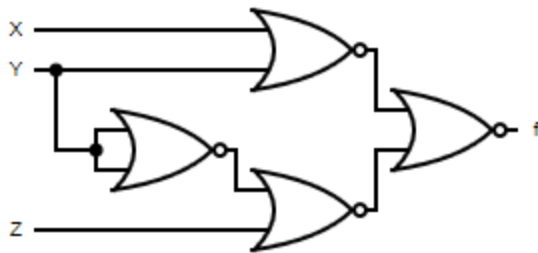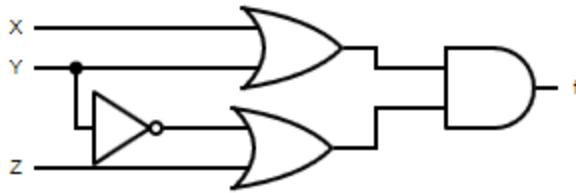2.7 Draw the circuit schematic for $f = (x + y)(\overline{y} + z)$ and then convert the schematic to NOR gates using the steps illustrated in the textbook.



2.8 Given $f = x\overline{y} + yz$ (an SOP expression) determine its equivalent POS expression. Hint: First find the SOP of \overline{f} and then use the rule “POS expression of f = Complement of the SOP expression of \overline{f} ”.

$$\begin{aligned} \overline{f} &= \overline{x}y + \overline{yz} \\ \text{SOP of } \overline{f} \quad \overline{f} &= (\overline{x} + y)(\overline{y} + \overline{z}) \\ \text{POS of} \quad f &= (x + \overline{y})(y + z) \end{aligned}$$

2.9 Obtain the POS expression of f by applying the Dual Principle to the SOP of \overline{f} where $f = x\overline{y} + yz$.

$$\begin{aligned} \overline{f} &= \overline{x}y + \overline{yz} \\ \text{dual of} \quad \overline{f} &= (\overline{x} + y)(\overline{y} + \overline{z}) \\ \text{POS of} \quad f &= (x + \overline{y})(y + z) \end{aligned}$$

2.10 Suppose we would like to build function $Y = 2X + 3$ where X denotes a 3-bit unsigned value $(x_2x_1x_0)_2$ and $Y = y_4y_3y_2y_1y_0$ is a 5-bit value in hardware. Construct its truth table where input bits are x_2, x_1 , and x_0 and output bits are y_4 through y_0 . Then do the following for output y_2 (you may repeat this for the other outputs):

x_2	x_1	x_0	y_4	y_3	y_2	y_1	y_0
0	0	0	0	0	0	1	1
0	0	1	0	0	1	0	1
0	1	0	0	0	1	1	1
0	1	1	0	1	0	0	1
1	0	0	0	1	0	1	1
1	0	1	0	1	1	0	1
1	1	0	0	1	1	1	1
1	1	1	1	0	0	0	1

a. Determine the canonical SOP expression for output bit y_2 .

$$y_2 = \overline{x_2}\overline{x_1}\overline{x_0} + \overline{x_2}\overline{x_1}x_0 + \overline{x_2}x_1\overline{x_0} + \overline{x_2}x_1x_0$$


b. Write the min-terms for y_2 .

$$f(x_1, x_0) = \sum(2, 1)$$

c. Use K-map and find a minimal SOP expression for y_2 .

$$y_2 = x_1\overline{x_0} + \overline{x_1}x_0$$

d. Draw a minimal NAND circuit for y_2 .

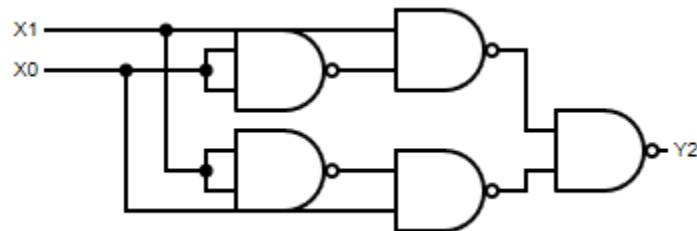

e. Compare the number of transistors required to implement the canonical and the minimal SOP expressions.

5 Transistors for minimal vs... upwards of 20 for canonical. Seems like minimal is a lot better

2.14 Find a minimal SOP expression for each of the following functions using K-maps:

a. $f(w, x, y, z) = \Sigma(0, 2, 8, 10) + \Sigma_d(12, 14)$

$$\begin{aligned} \text{Canonical SOP: } f &= (\overline{w}xyz + \overline{w}x\overline{y}z + w\overline{x}yz + w\overline{x}\overline{y}z) + (wx\overline{y}z + wx\overline{y}\overline{z}) \\ &= ((\overline{w}xz)(\overline{y} + y) + (w\overline{x}z)(\overline{y} + y)) + ((wx\overline{z})(\overline{y} + y)) \\ &= ((\overline{w}xz) + (w\overline{x}z)) + (wx\overline{z}) \rightarrow (\overline{x}z) + (wx\overline{z}) \end{aligned}$$

Minimal SOP: $f = (\overline{x}z) + (wx\overline{z})$ Error! Bookmark not defined.

b. $g(a, b, c, d) = \Sigma(5, 7, 13, 15) + \Sigma_d(6, 14)$

$$\begin{aligned} \text{Canonical SOP: } g &= (\overline{a}b\overline{c}d + \overline{a}bcd + ab\overline{c}d + abcd) + (\overline{a}bc\overline{d} + abc\overline{d}) \\ &= ((\overline{a}bd)(c + \overline{c}) + (abd)(c + \overline{c})) + ((bc\overline{d})(a + \overline{a})) \\ &= (\overline{a}bd) + (abd) + (bc\overline{d}) \rightarrow (bd) + (bc\overline{d}) \end{aligned}$$

Minimal SOP: $g = (bd) + (bc\overline{d})$

c. $h(w, x, y, z) = \Pi(0, 2, 8, 10) + \Pi_d(12, 14)$

$$\begin{aligned} \text{Canonical SOP: } h &= (\overline{w}xyz + \overline{w}x\overline{y}z + w\overline{x}yz + w\overline{x}\overline{y}z) + (wx\overline{y}z + wx\overline{y}\overline{z}) \\ &= ((\overline{w}xz)(\overline{y} + y) + (w\overline{x}z)(\overline{y} + y)) + ((wx\overline{z})(\overline{y} + y)) \\ &= ((\overline{w}xz) + (w\overline{x}z)) + (wx\overline{z}) \rightarrow (\overline{x}z) + (wx\overline{z}) \end{aligned}$$

Minimal SOP: $h = (\overline{x}z) + (wx\overline{z})$ Error! Bookmark not defined.

d. $t(a, b, c, d) = \Pi(5, 7, 13, 15) + \Pi_d(6, 14)$

$$\begin{aligned} \text{Canonical SOP: } t &= (\overline{a}b\overline{c}d + \overline{a}bcd + ab\overline{c}d + abcd) + (\overline{a}bc\overline{d} + abc\overline{d}) \\ &= ((\overline{a}bd)(c + \overline{c}) + (abd)(c + \overline{c})) + ((bc\overline{d})(a + \overline{a})) \\ &= (\overline{a}bd) + (abd) + (bc\overline{d}) \rightarrow (bd) + (bc\overline{d}) \end{aligned}$$

Minimal SOP: $t = (bd) + (bc\overline{d})$

2.15 Find minimal POS expressions for each of the functions given in Problem 2.14.

a. Minimal POS: $f = (w+y+z)(w+\overline{x}+\overline{y}+\overline{z})(\overline{z})$

b. Minimal POS: $g = (a+\overline{b}+d)(\overline{d})$

c. Minimal POS: $h = (w+y+z)(w+\overline{x}+\overline{y}+\overline{z})(\overline{z})$

d. Minimal POS: $t = (a+\overline{b}+d)(\overline{d})$